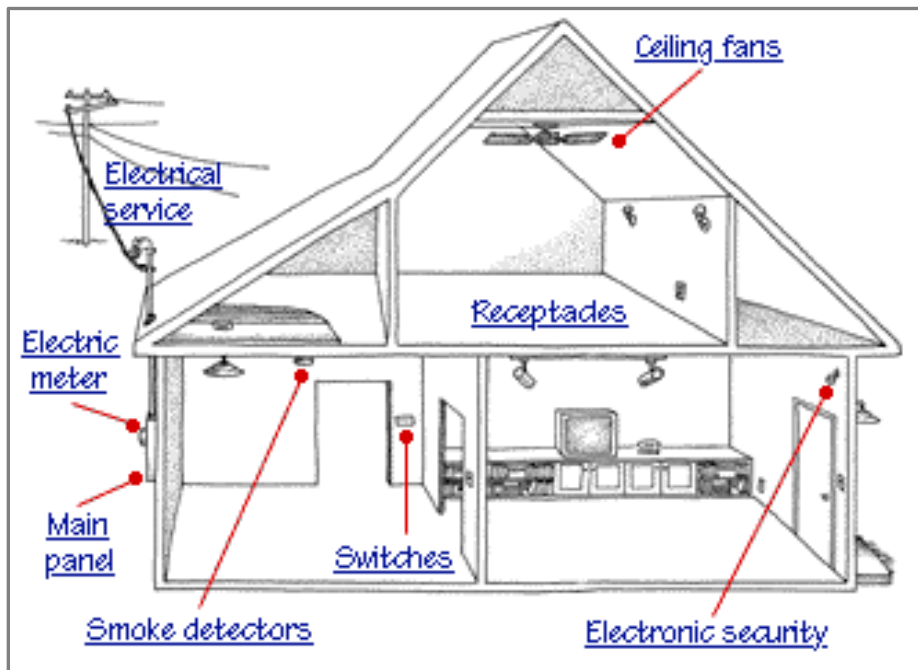



# Faculty of Engineering

## ENGR 311: System Dynamics
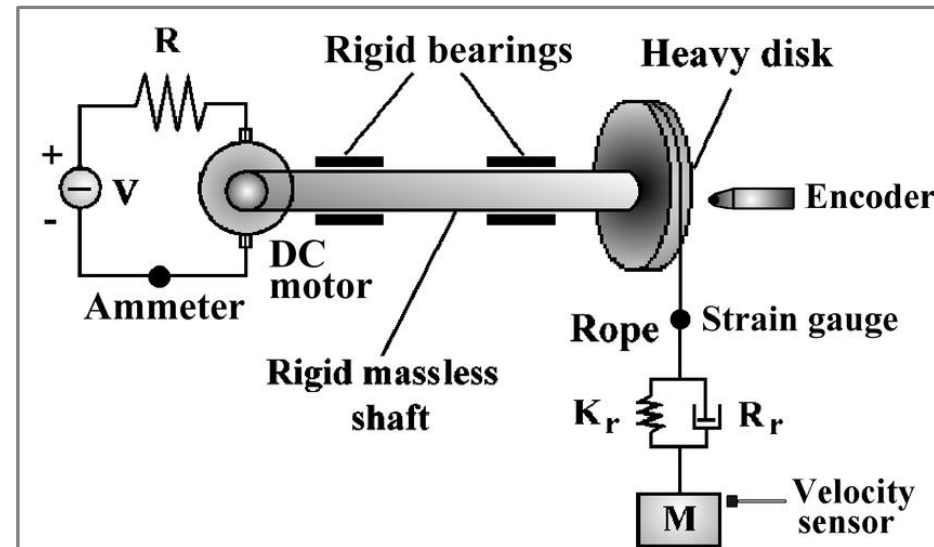
### Fall 2020



<https://www.hometips.com/how-it-works/electrical-panel-circuit-breakers.html>



[https://www.researchgate.net/figure/An-electromechanical-system-with-its-instrumentation\\_fig36\\_257351591](https://www.researchgate.net/figure/An-electromechanical-system-with-its-instrumentation_fig36_257351591)

## Chapter 7

30/11/2020


# Electrical and Electromechanical Systems

# Outline

- ❑ Introduction
- ❑ Fundamental of Electrical Circuits
- ❑ Mathematical Modeling of Electrical Systems
- ❑ ~~Analogous Systems~~
- ❑ ~~Mathematical Modeling of Electromechanical Systems~~

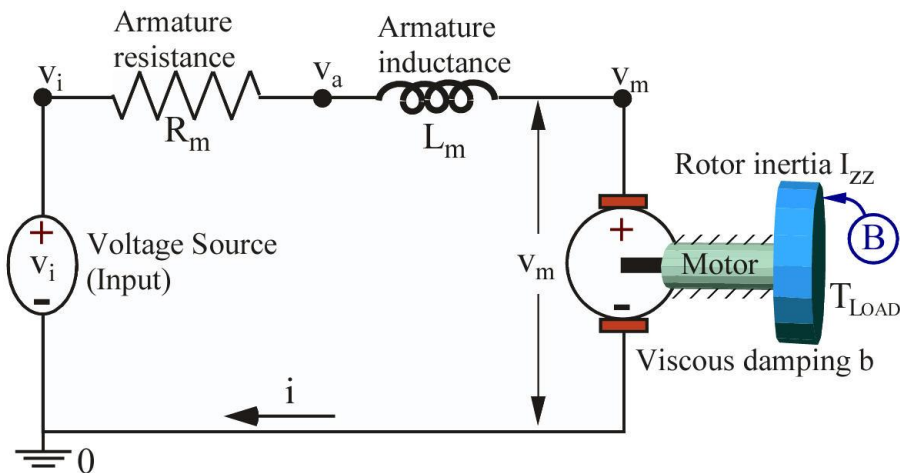
# Introduction

- The majority of engineering systems now have at least one electrical subsystem.
- This may be a power supply, sensor, motor, controller, or an acoustic device such as a speaker. So an understanding of electrical systems is essential to understanding the behavior of many systems.
- Electrical systems permit us to easily transmit energy from a source of supply to a point of application.



<http://www.motiongenesis.com/MGWebSite/MGGetStarted/MGExampleDCMotorWithRLCircuit/MGExampleMotorWithRLCircuit.html>

Electromechanical: Simple DC motor

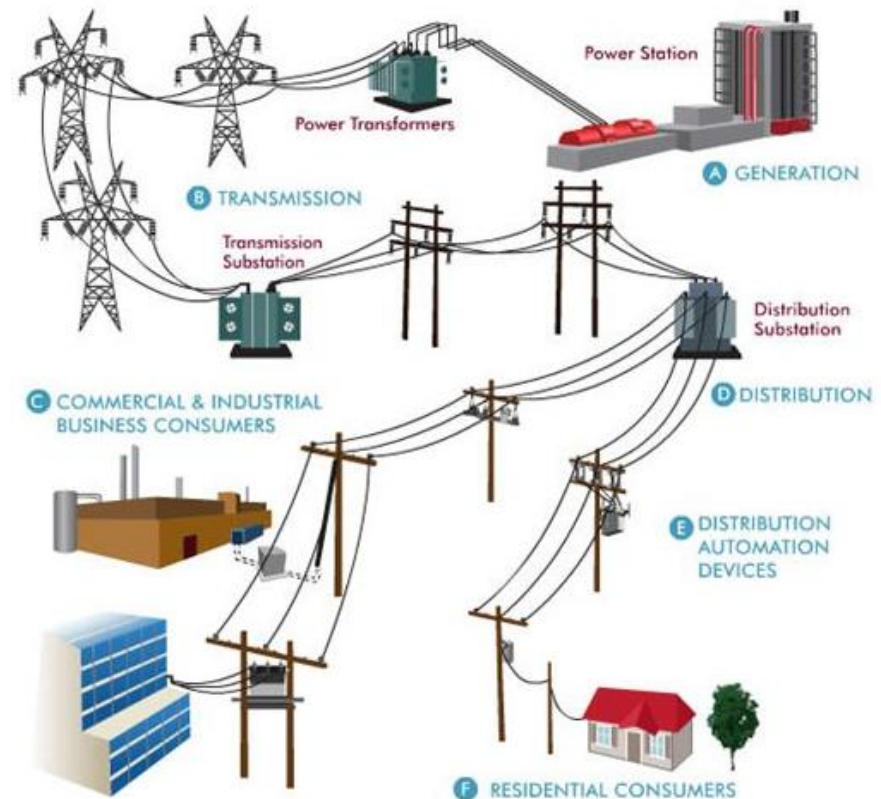

<https://slideplayer.com/slide/5872983/>

Basic of electrical system

# Introduction


## Electrical Elements: Energy Sources

- An active two-terminal element that supplies energy to a circuit is a source of energy.
- A voltage source is a two-terminal device that causes a specified voltage to exist between two points in a circuit. The voltage may be time varying or time invariant (for a sufficiently long time). Examples include batteries and generators.
- An ideal voltage source maintains a fixed voltage drop across its terminals, independent of the load resistance or the output current.
- A current source causes a specified current to flow through a wire containing this source. Example is transistor current source.
- An ideal current source is a circuit element that maintains a prescribed current through its terminals regardless of the voltage across those terminals.




<http://carunderstanding.com/how-to-charge-rv-battery-with-generator/>


### Generator and Battery

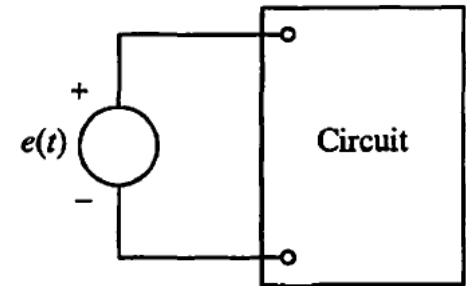

### Voltage Source

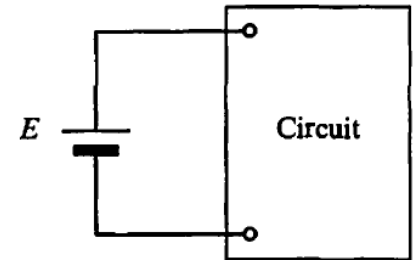

### Time Invariant Voltage source

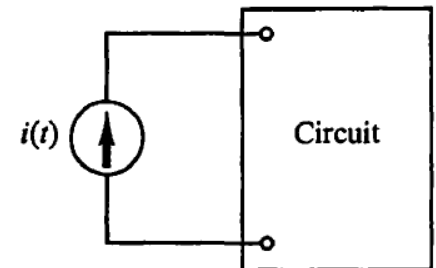


### Current Source

# Introduction
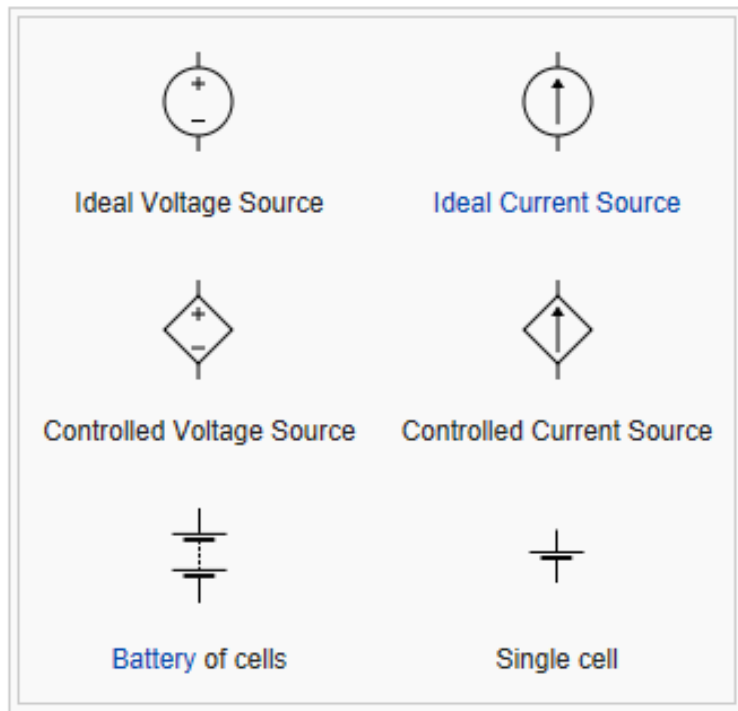
## Electrical Elements: Energy Sources



- These circuit elements do not exist as practical devices. A real-world voltage source cannot supply unlimited current. A voltage source is the dual of a current source.



[https://en.wikipedia.org/wiki/Voltage\\_source](https://en.wikipedia.org/wiki/Voltage_source)
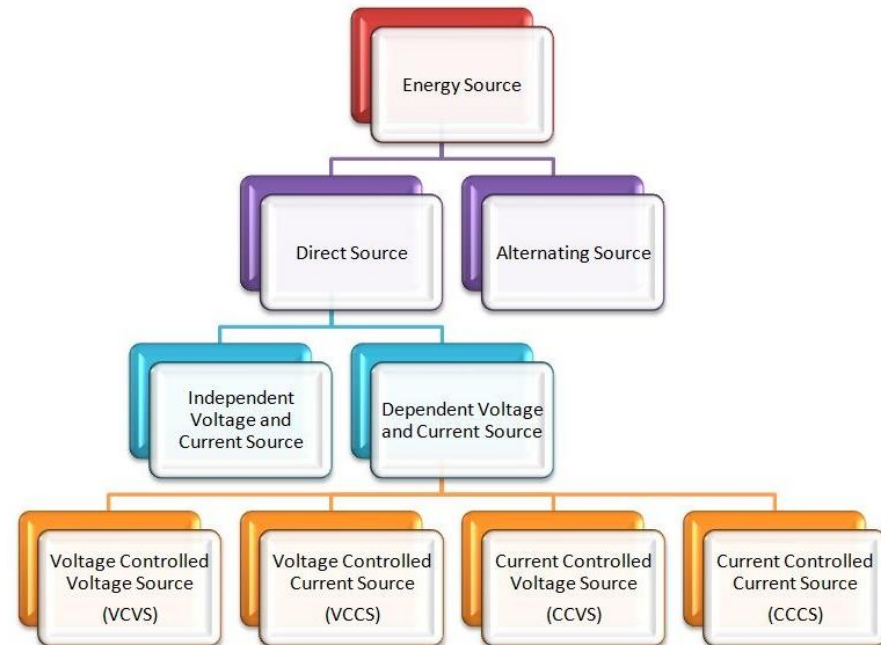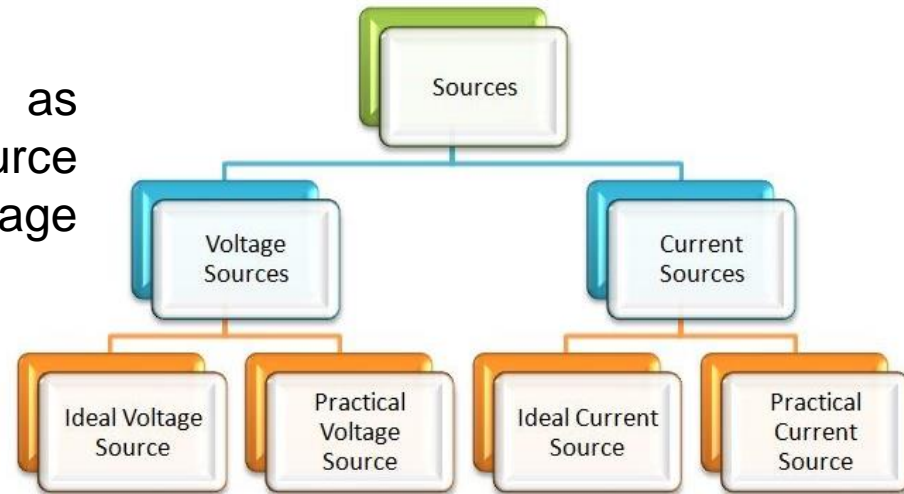
### Symbols used for voltage and current sources

- Voltage and current are the primary variables used to describe a circuit's behavior.



<https://circuitglobe.com/independent-dependent-voltage-and-current-source.html>

### Circuit Energy Sources

# Introduction


## Electrical Elements: Current and Voltage

- Current is the flow of electrons. It is the time rate of change of electrons passing through a defined area, such as the cross section of a wire. Because electrons are negatively charged, the positive direction of current flow is opposite to that of the electron flow.
- The mathematical description of the relation between the number of electrons (called charge  $Q$ ) and current  $i$  is

$$i = \frac{dQ}{dt}$$


or

$$Q(t) = \int i dt$$

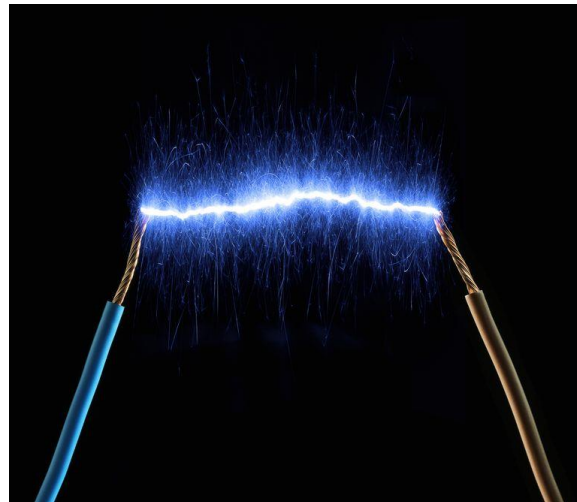

<https://www.thoughtco.com/electrical-current-2698954>

Electrical current

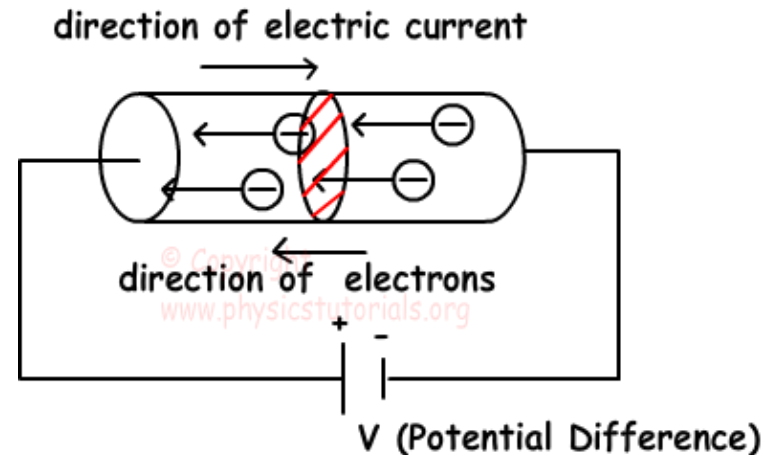

<http://www.physicstutorials.org/home/electric-current/electric-current-and-flow-of-charge>


Electrical current and flow of charge

- The unit of charge is the coulomb (C), and the unit of current is the ampere (A), which is one coulomb per second. These units, and the others we will use for electrical systems, are the same in both the SI and FPS systems.

# Introduction
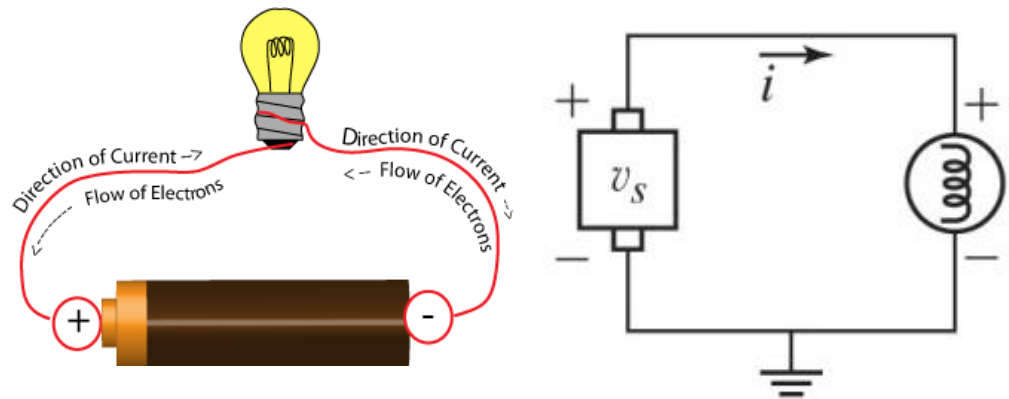
## Electrical Elements: Current and Voltage

- Energy is required to move a charge between two points in a circuit. The work per unit charge required to do this is called voltage. The unit of voltage is the volt (V), which is defined to be one joule per coulomb.
- The sign of voltage difference is important. The Figure shows a battery connected to a lightbulb. The electrons in the wire are attracted to the battery's positive terminal; thus the positive direction of current is clockwise, as indicated by the arrow.
- Because the battery supplies energy to move electrons and the lightbulb dissipates energy (through light and heat), the sign of voltage difference across the battery is the opposite of the sign of the voltage difference across the lightbulb.



A battery-lightbulb circuit



# Introduction

## Electrical Elements: Resistor


- The bulb current depends on the voltage difference and the bulb's material properties, which resist the current and cause the energy loss.
- When a current flows through wire or other circuit elements, it encounters resistance. Sometimes this resistance is desirable and intentionally introduced; sometimes not.
- A resistor is an element designed to provide resistance. Most resistors are designed to have a linear relation between the current passing through them and the voltage difference across them. This linear relation is Ohm's law. It states that

$$v = iR$$


or

$$R = \frac{v}{i}$$

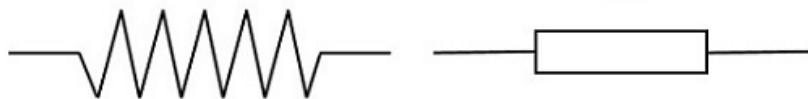where  $i$  is the current,  $v$  is the voltage difference, and  $R$  is the resistance. The unit of resistance is the ohm ( $\Omega$ ), which is one volt per ampere.



Symbol for a fixed resistor

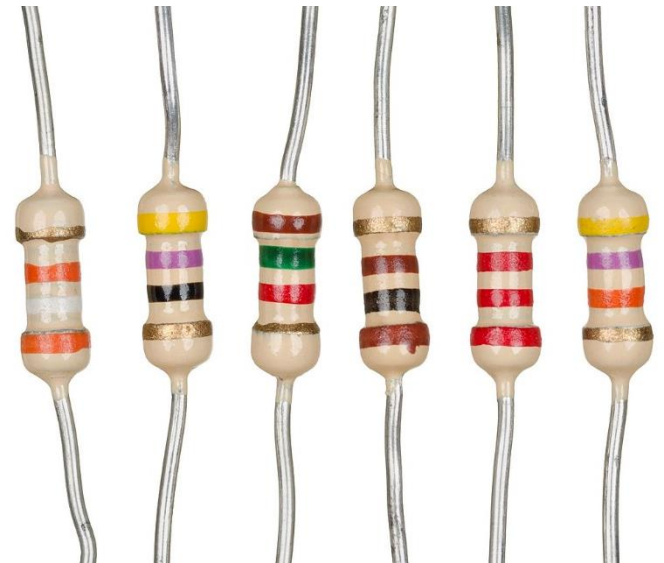


<https://en.wikipedia.org/wiki/Resistor>

An array of axial-lead resistor



# Introduction

## Electrical Elements: Resistor

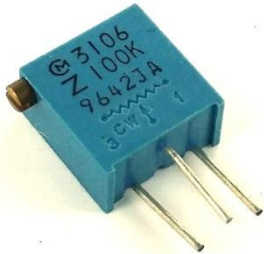

<https://www.westfloridacomponents.com/P178PD/100K+ohm+Variable+Resistor+Trimpot++POT3106Z-1-104+3106Z-1-104.html>




<https://www.lelong.com.my/potentiometer-variable-resistor-50k-ohm-realove-F745807-2007-01-Sale-1.htm>



<http://www.edubilla.com/invention/variable-resistor/>
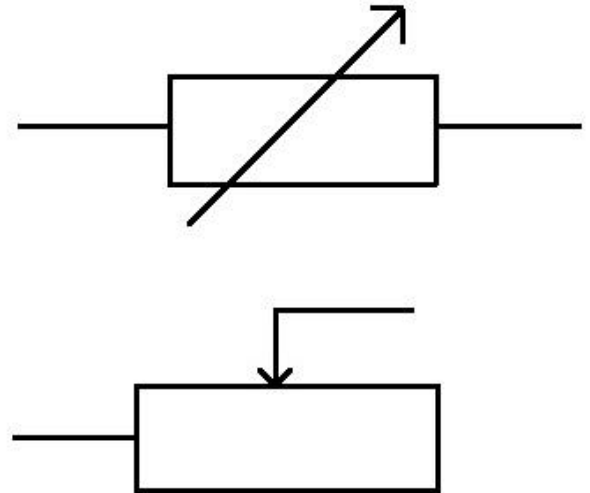
### Variable Resistors: Potentiometer/Rheostat




Symbol for a variable resistor

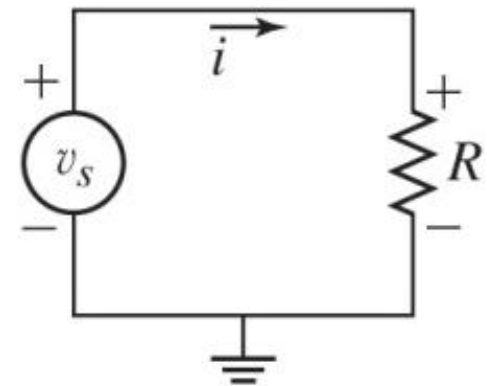- Example, because of conservation of energy, the voltage increase  $v_s$  supplied by the source must equal the voltage drop  $iR$  across the resistor. Thus the model of this circuit is

$$v_s = iR$$

- Resistors do not store electric energy in any form, but instead dissipate it as heat. Note that real resistors may not be linear and may also exhibit some capacitance and inductance effects.





Circuit diagram representation of the battery-lightbulb circuit

# Introduction
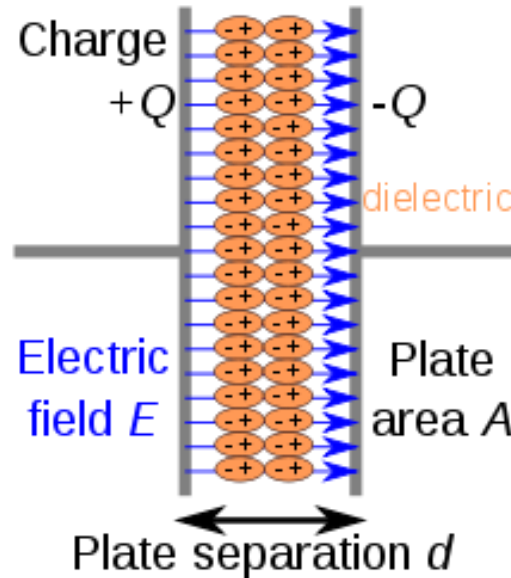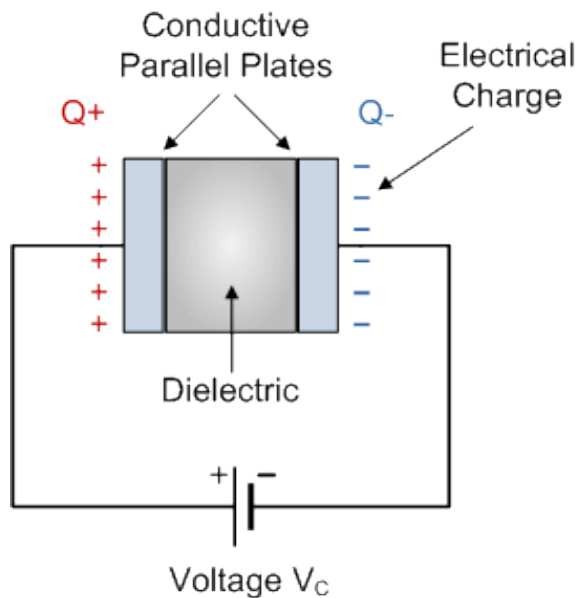
## Electrical Elements: Capacitor


- Two conductors separated by a nonconducting medium form a capacitor, so two metallic plates separated by a very thin dielectric material (glass, air, paper, plastic, ceramic, etc.) form a capacitor.




<https://en.wikipedia.org/wiki/Capacitor>
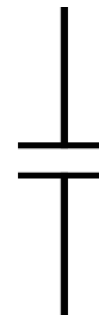
### Capacity


Charge separation in a parallel-plate capacitor causes an internal electric field. A dielectric (orange) reduces the field and increases the capacitance



Fixed Capacitor

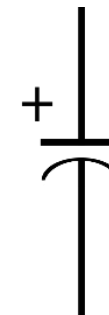

Polarized Capacitor

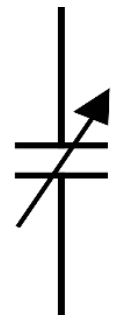

Variable Capacitor

### Symbol for a capacity

# Introduction

## Electrical Elements: Capacitor

- The capacitance is a measure of the quantity of charge that can be stored for a given voltage across the plates.
- An ideal (pure) capacitor is characterized by a constant capacitance  $C$ , in farads (F) in the SI system of units, defined as the ratio of the positive or negative charge  $Q$  on each conductor to the voltage  $V$  between them.

$$\boxed{v = \frac{Q}{C}} \quad \text{and} \quad \boxed{i = \frac{dQ}{dt}} \quad \rightarrow \quad \boxed{i = C \frac{dv}{dt}}$$

- Thus,
  - The unit of capacitance is the farad (F).

$$\boxed{v(t) = \frac{1}{C} \int i dt = \frac{1}{C} \int_0^t i dt + \frac{Q_o}{C}} \quad \text{or} \quad \boxed{v(t) = \frac{1}{C} \int_0^t i dt + v(0)}$$

where  $Q_o$  is the initial charge on the capacitor at time  $t = 0$ .

- Although a pure capacitor stores energy and can release all of it, real capacitors exhibit various losses. These energy losses are indicated by a power factor, which is the ratio of the energy lost per cycle of ac voltage to the energy stored per cycle. Thus, a small-valued power factor is desirable.


# Introduction

## Electrical Elements: Inductor

- A magnetic field (a flux) surrounds a moving charge or current. If the conductor of the current is coiled, the flux created by the current in one loop affects the adjacent loops.
- If a circuit lies in a time-varying magnetic field, an electromotive force is induced in the circuit. The inductive effects can be classified as self-inductance and mutual inductance.
- If the circuit does not contain ferromagnetic elements (such as an iron core), the rate of change of flux is proportional to  $di/dt$ .

$$\Phi = Li$$

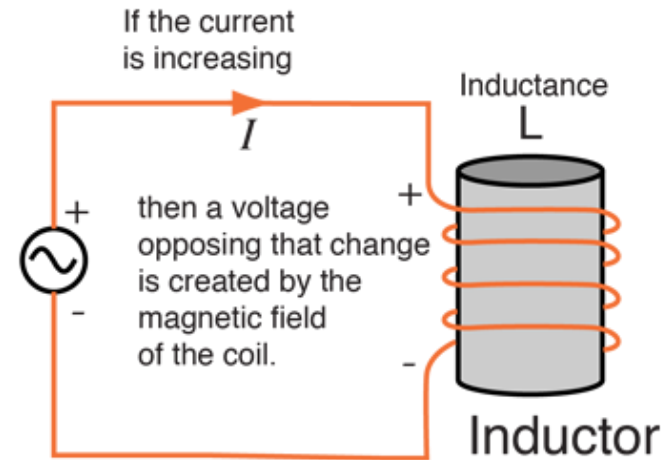where  $L$  is the inductance and  $\Phi$  is the flux across the inductor.



<http://hyperphysics.phy-astr.gsu.edu/hbase/electric/induct.html>

Inductor



<https://www.miniphysics.com/uy1-self-inductance-inductors.html>

Coil Inductance

# Introduction

## Electrical Elements: Inductor

- And the flux is proportional to the time integral of the applied voltage.

$$\phi = \int v dt$$

- For self-inductance, or simply inductance, we have

$$i = \frac{1}{L} \int v dt$$

or

$$v = L \frac{di}{dt}$$

- Thus,
  - The unit of inductance is the henry (H).

$$i(t) = \frac{1}{L} \int_0^t v dt + i(0)$$

or

$$i(t) = \frac{1}{L} \int_0^t v dt + \frac{\phi_o}{L}$$

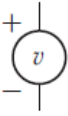

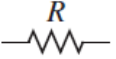
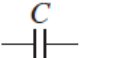
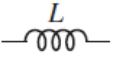
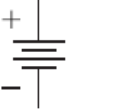

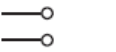
where  $\phi_o$  is the initial flux across the inductor at time  $t = 0$ .

- Because most inductors are coils of wire, they have considerable resistance. The energy loss due to the presence of resistance is indicated by the quality factor  $Q$ , which denotes the ratio of stored to dissipated energy. A high value of  $Q$  generally means that the inductor contains small resistance.

# Introduction


## Electrical Elements: Active and Passive

- Circuit elements may be classified as active or passive.
- Passive elements such as resistors, capacitors, and inductors are not sources of energy, although the latter two can store it temporarily.
- Elements that provide energy are sources, and elements that dissipate energy are loads.
- The active elements are energy sources that drive the system. There are several types available; for example, chemical (batteries), mechanical (generators), thermal (thermocouples), and optical (solar cells).
- Active elements are modeled as either ideal voltage sources or ideal current sources.


Electrical quantities		
Quantity	Units	Circuit symbol
Voltage	volt (V)	Voltage Source 
Charge	coulomb (C) = N · m/V	Current Source 
Current	ampere (A) = C/s	
Resistance	ohm ( $\Omega$ ) = V/A	
Capacitance	farad (F) = C/V	
Inductance	henry (H) = V · s/A	
Battery	—	
Ground	—	
Terminals (input or output)	—	

# Fundamentals of Electrical Circuits

## Ohm's Law

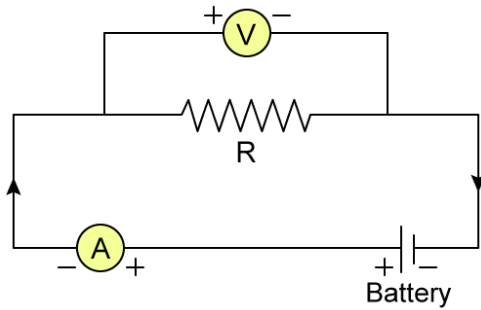


$$v = iR$$

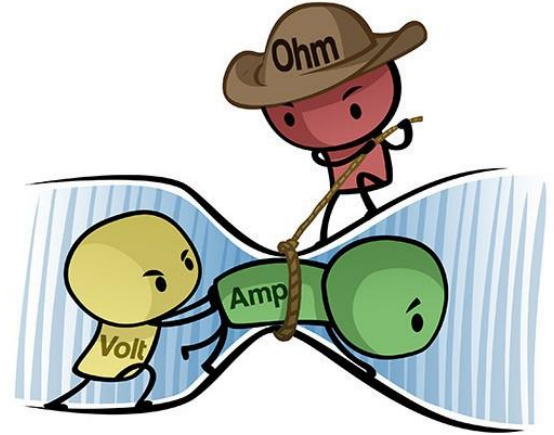


<https://www.build-electronic-circuits.com/ohms-law/>

## Series Resistance

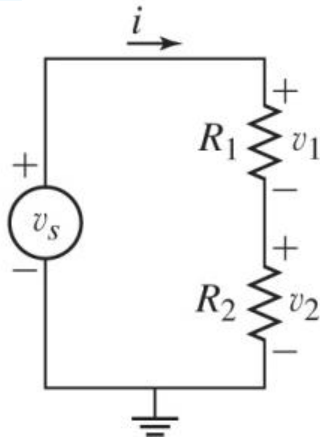

$$R_T = R_e = R = R_1 + R_2$$

## Parallel Resistance

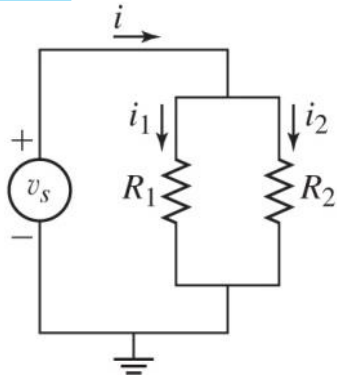

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2}$$

or

$$R = \frac{R_1 R_2}{R_1 + R_2}$$




# Fundamentals of Electrical Circuits


## Example 1

(a) Determine the combined resistance  $R$ .


(i)

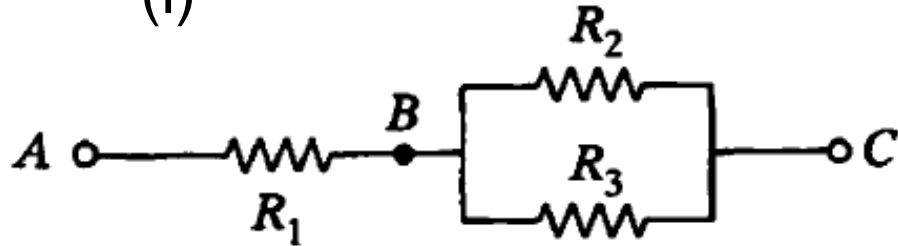


(ii)

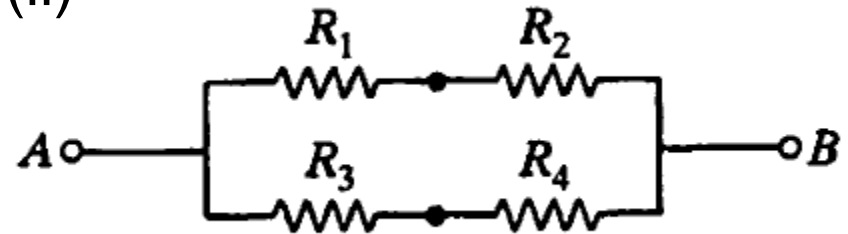

(iii)

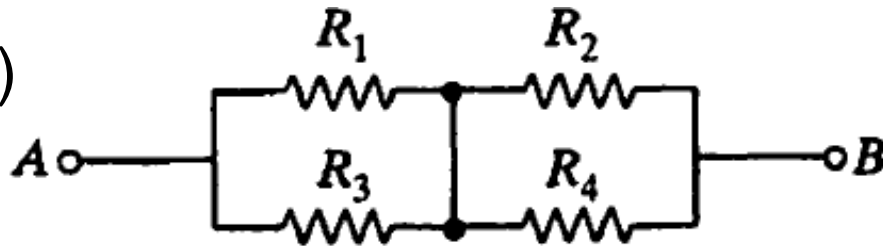

(b) Determine the current  $I_1$ .

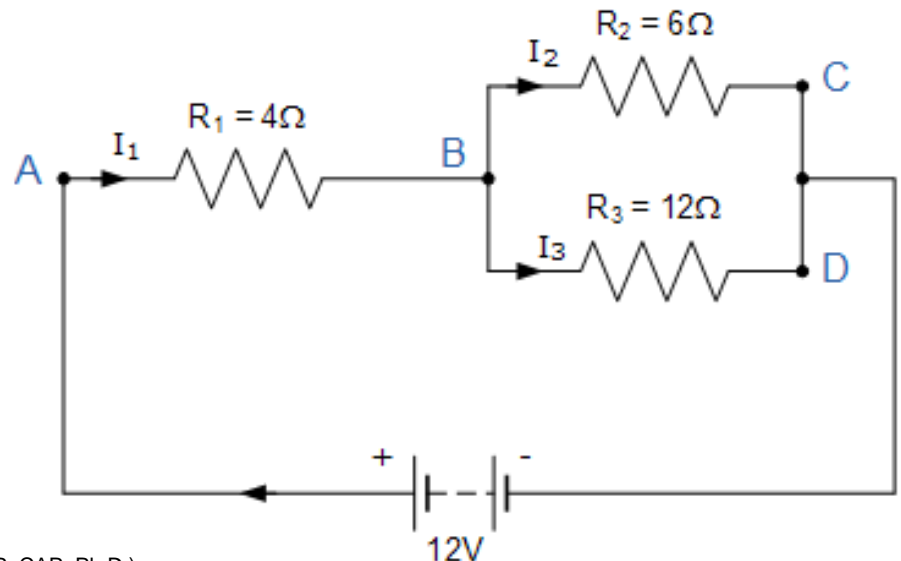


# Fundamentals of Electrical Circuits

## Kirchhoff's Law

- In solving circuit problems that involve many electromotive forces, resistances, capacitances, inductances, and so on, it is often necessary to use Kirchhoff's laws, of which there are two: the current law (node law) and the voltage law (loop law).
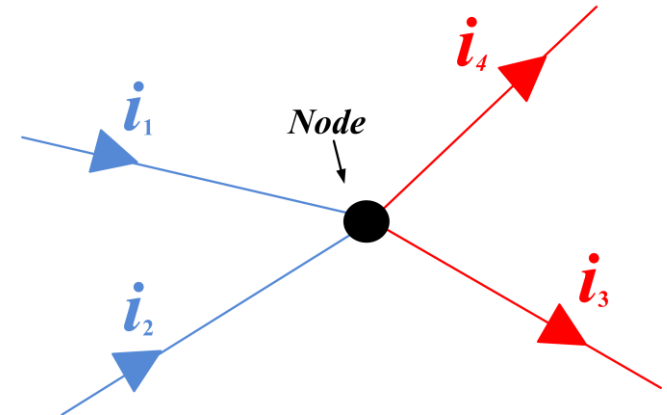
## Kirchhoff's Current Law

- A basic law used to model electrical systems using conservation of charge.
- A node in an electrical circuit is a point where three or more wires are joined together.
- The law states that the algebraic sum of all currents entering and leaving a node is zero. (This law can also be stated as follows: The sum of all the currents entering a node is equal to the sum of all the currents leaving the same node.)
- Conversion: Currents going toward a node should be preceded by a plus sign; currents going away from a node should be preceded by a minus sign.



$$i_1 + i_2 - i_3 - i_4 = 0$$





or

$$i_1 + i_2 = i_3 + i_4$$

# Fundamentals of Electrical Circuits
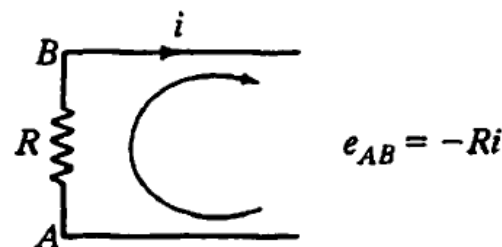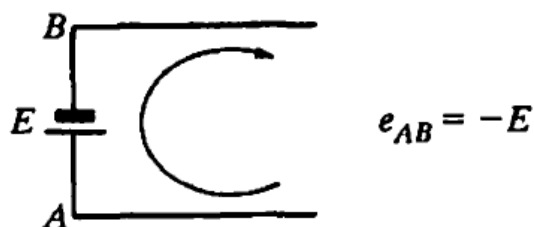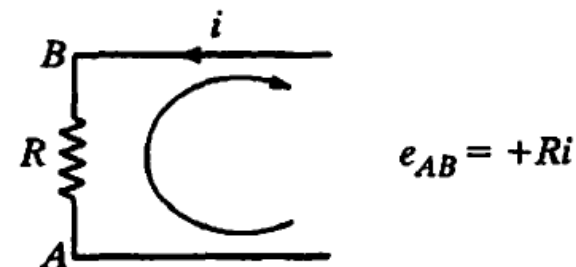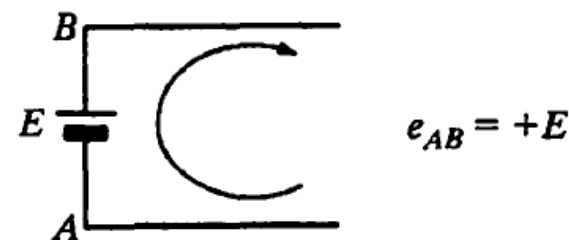
## Kirchhoff's Voltage Law

- This basic law uses conservation of energy.
- Kirchhoff's voltage law states that at any given instant of time the algebraic sum of the voltages around any loop in an electrical circuit is zero: The sum of the voltage drops is equal to the sum of the voltage rises around a loop.
- Conversion: A rise in voltage [which occurs in going through a source of electromotive force from the negative to the positive terminal, or in going through a resistance in opposition to the current flow] should be preceded by a plus sign.
- Conversion: A drop in voltage [which occurs in going through a source of electromotive force from the positive to the negative terminal, or in going through a resistance in the direction of the current flow] should be preceded by a minus sign.




# Fundamentals of Electrical Circuits

## Example 2

Obtain the mathematical model of the following circuits.


(a)

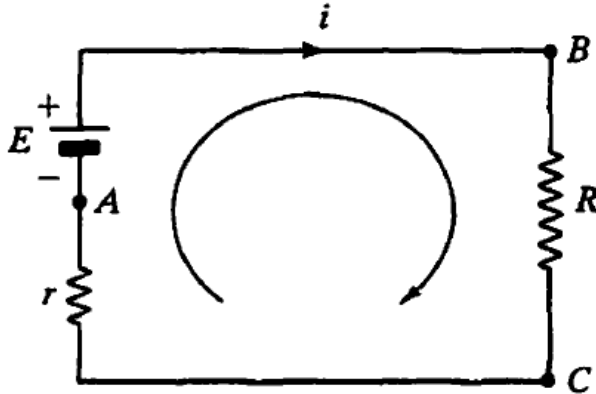

$$E - iR - ir = 0 \quad \text{Or} \quad E = iR + ir$$


$$i = \frac{E}{R + r}$$

(b)

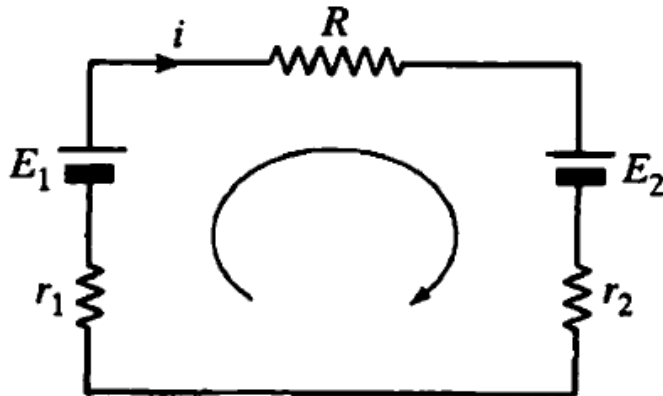

$$E_1 - iR - E_2 - ir_2 - ir_1 = 0$$

$$i = \frac{E_1 - E_2}{r_1 + r_2 + R}$$

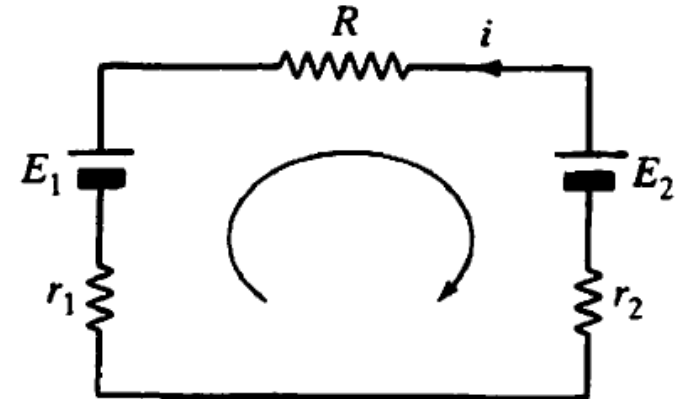

$$E_1 + iR - E_2 + ir_2 + ir_1 = 0$$


$$i = \frac{E_2 - E_1}{r_1 + r_2 + R}$$

# Fundamentals of Electrical Circuits

## Example 2

Obtain the mathematical model of the following circuits.

(c)

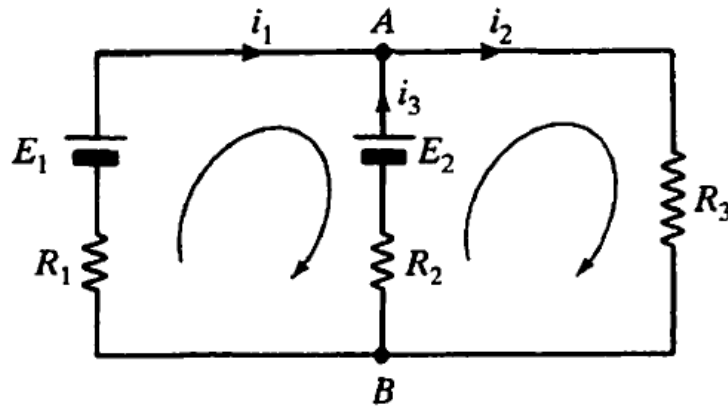


**KCL:**

At point A:  $i_1 + i_3 - i_2 = 0$

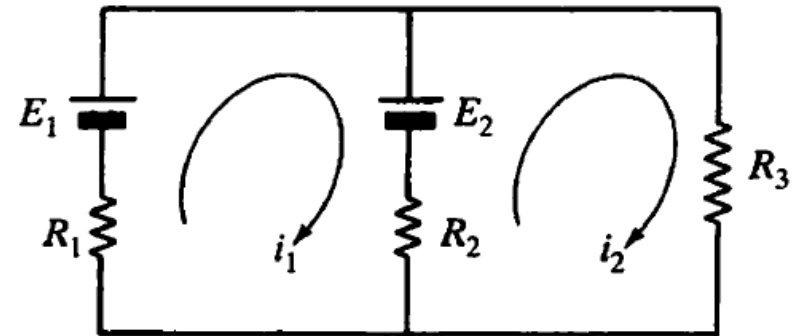**KVL:**

Left loop:  $E_1 - E_2 + i_3 R_2 - i_1 R_1 = 0$

Right loop:  $E_2 - i_2 R_3 - i_3 R_2 = 0$



**KVL:**

Left loop:

$$E_1 - E_2 - R_2(i_1 - i_2) - R_1 i_1 = 0$$

Right loop:

$$E_2 - R_3 i_2 - R_2(i_2 - i_1) = 0$$



$$i_3 = \frac{E_1(R_1 + R_3) - E_1 R_3}{R_1 R_2 + R_2 R_3 + R_3 R_1} \quad i_1 = \frac{E_1(R_2 + R_3) - E_2 R_3}{R_1 R_2 + R_2 R_3 + R_3 R_1} \quad i_2 = \frac{E_1 R_2 + E_2 R_1}{R_1 R_2 + R_2 R_3 + R_3 R_1}$$

# Mathematical Modeling of Electrical Systems

- The first step in analyzing circuit problems is to obtain mathematical models for the circuits. (Although the terms circuit and network are sometimes used interchangeably, network implies a more complicated interconnection than circuit.)
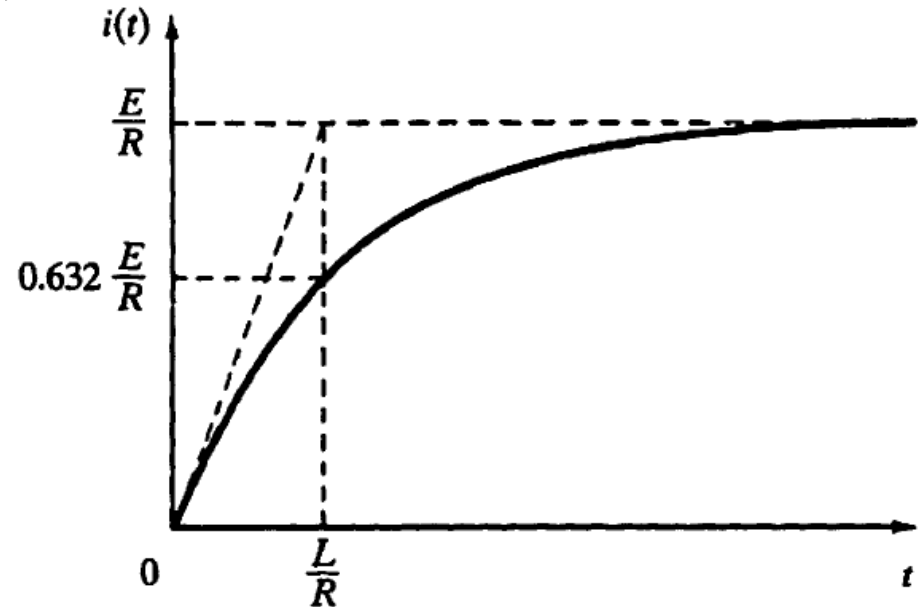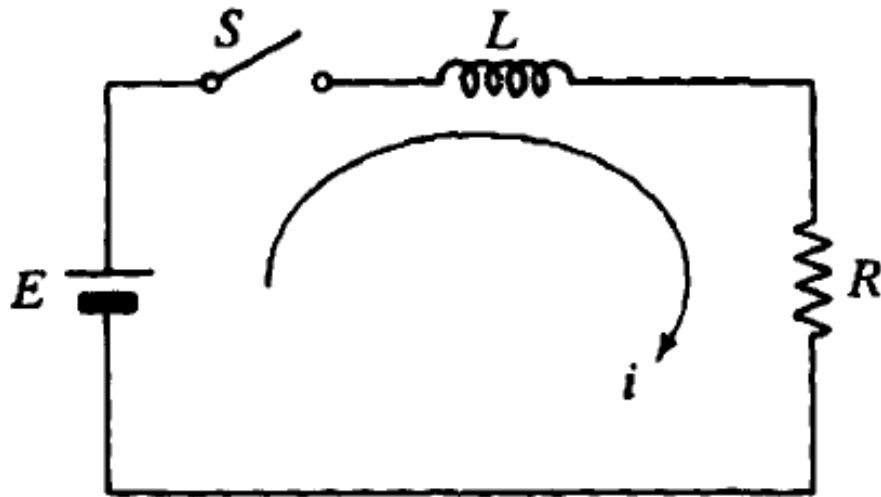
## First-order Systems: Illustration 1

- Consider the circuit shown in the Figure. Assume that the switch  $S$  is open for  $t < 0$  and closed at  $t = 0$ . Obtain a mathematical model for the circuit and obtain an equation for the current  $i(t)$ .



$$L \frac{di}{dt} + Ri = E \quad i(0) = 0$$

$$i(t) = \frac{E}{R} [1 - e^{-(R/L)t}]$$


# Mathematical Modeling of Electrical Systems

## First-order Systems: Illustration 2

- Consider again the circuit shown in the Figure. Assume that switch  $S$  is open for  $t < 0$ , it is closed at  $t = 0$ , and is open again at  $t = t_1 > 0$ . Obtain a mathematical model for the system, and find the current  $i(t)$  for  $t \geq 0$ .


$$L \frac{di}{dt} + Ri = E \quad i(0) = 0 \quad 0 \leq t < t_1$$
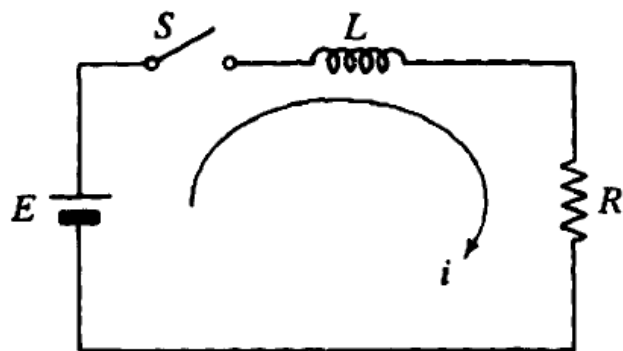
$$L \frac{di}{dt} + Ri = 0 \quad i(t_1) = \frac{E}{R} [1 - e^{-(R/L)t_1}] \quad t \geq t_1$$



$$i(t) = \frac{E}{R} [1 - e^{-(R/L)t}], \quad 0 \leq t < t_1$$
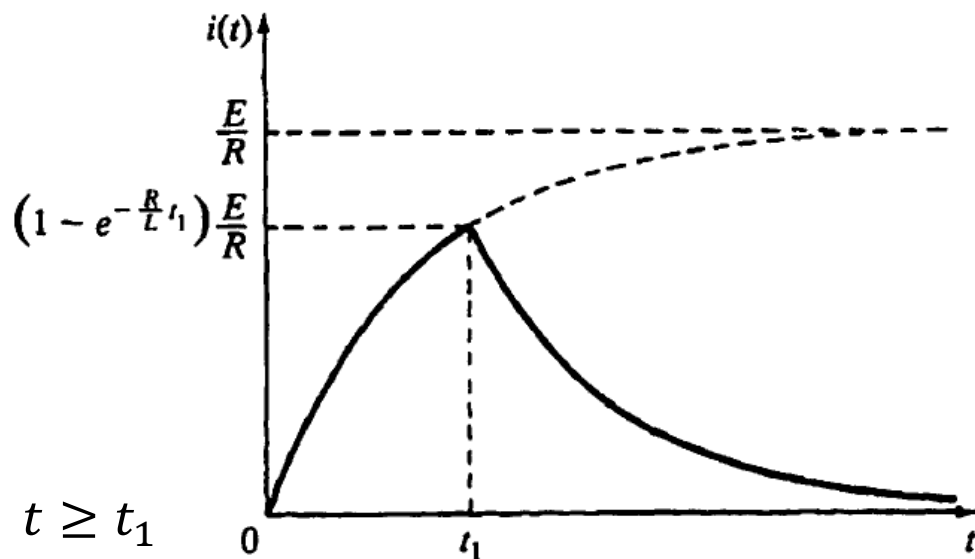
$$= \frac{E}{R} [1 - e^{-(R/L)t_1}] e^{-(R/L)(t-t_1)}, \quad t \geq t_1$$






## Mathematical Modeling of Electrical Systems
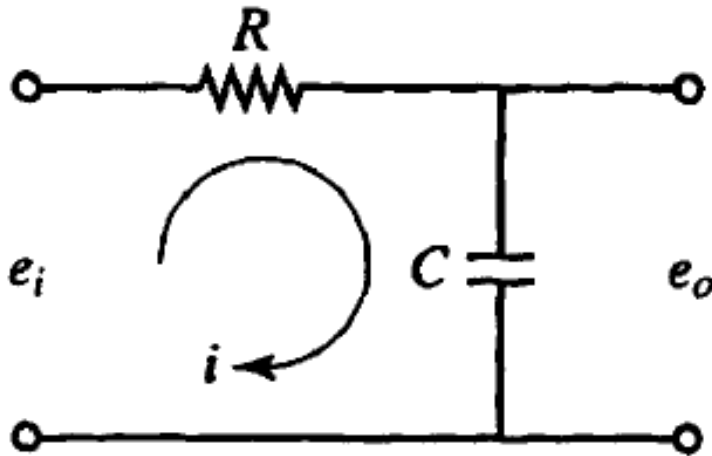
### First-order Systems: Illustration 3

- Consider the electrical circuit shown in the Figure. The circuit consists of a resistance  $R$  (in ohms) and a capacitance  $C$  (in farads). Obtain the transfer function  $E_o(s)/E_i(s)$ . Also, obtain a state-space representation of the system.



$$Ri + \frac{1}{C} \int i dt = e_i$$

$$\frac{1}{C} \int i dt = e_o \quad \text{or} \quad i = C \frac{de_o}{dt}$$

$$\frac{E_o(s)}{E_i(s)} = \frac{1}{RCs + 1}$$

$$RC \frac{de_o}{dt} + e_o = e_i$$

$$\text{Or} \quad RC \dot{e}_o + e_o = e_i$$

$$x = e_o$$

$$u = e_i$$

$$y = e_o = x$$

$$\dot{x} = -\frac{1}{RC}x + \frac{1}{RC}u$$

$$y = x$$

$$A = -\frac{1}{RC}$$

$$B = \frac{1}{RC}$$


$$C = 1$$

$$D = 0$$

# Mathematical Modeling of Electrical Systems
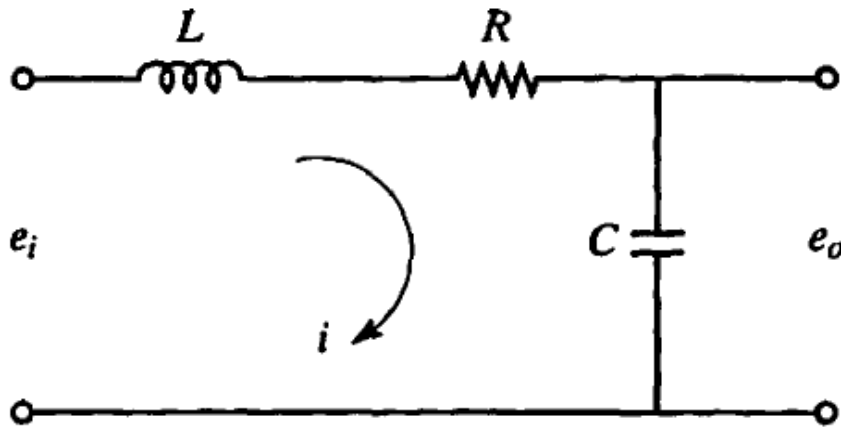
## Second-order Systems: Illustration 1

- Consider the electrical circuit shown in the Figure. The circuit consists of an inductance  $L$  (in henrys), a resistance  $R$  (in ohms), and a capacitance  $C$  (in farads). Obtain the transfer function  $E_o(s)/E_i(s)$ . Also, obtain a state-space representation of the system.



$$L \frac{di}{dt} + Ri + \frac{1}{C} \int i dt = e_i$$

$$\frac{1}{C} \int i dt = e_o \quad \text{or} \quad i = C \frac{de_o}{dt}$$

$$\frac{E_o(s)}{E_i(s)} = \frac{1}{LCs^2 + RCs + 1}$$

$$\ddot{e}_o + \frac{R}{L} \dot{e}_o + \frac{1}{LC} e_o = \frac{1}{LC} e_i$$

$$x_1 = e_o$$

$$x_2 = \dot{e}_o$$

$$u = e_i$$

$$y = e_o = x_1$$


$$\begin{bmatrix} \dot{x}_1 \\ \dot{x}_2 \end{bmatrix} = \begin{bmatrix} 0 & 1 \\ -\frac{1}{LC} & -\frac{R}{L} \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \end{bmatrix} + \begin{bmatrix} 0 \\ \frac{1}{LC} \end{bmatrix} u$$

$$y = [1 \quad 0] \begin{bmatrix} x_1 \\ x_2 \end{bmatrix}$$


# Mathematical Modeling of Electrical Systems
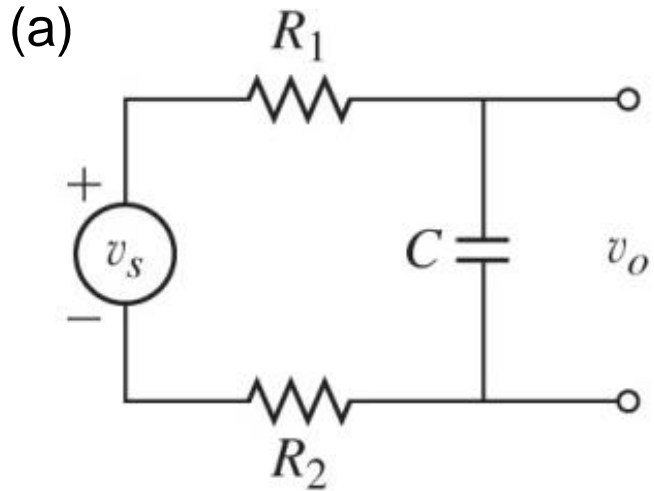
## Example 3


Obtain the model of the voltage  $v_o$ , given the supply voltage  $v_s$  for the circuits shown below.


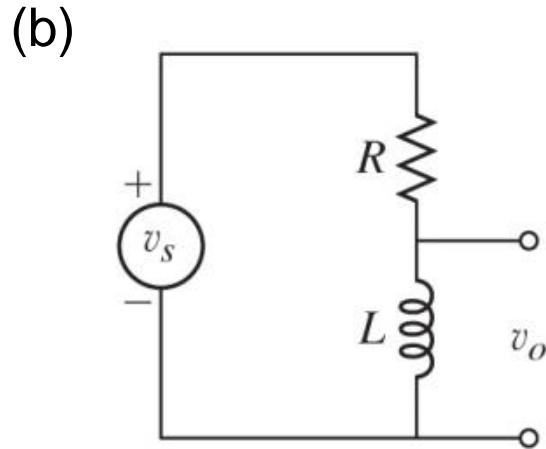
$$(R_1 + R_2)C \frac{dv_o}{dt} + v_o = v_s$$


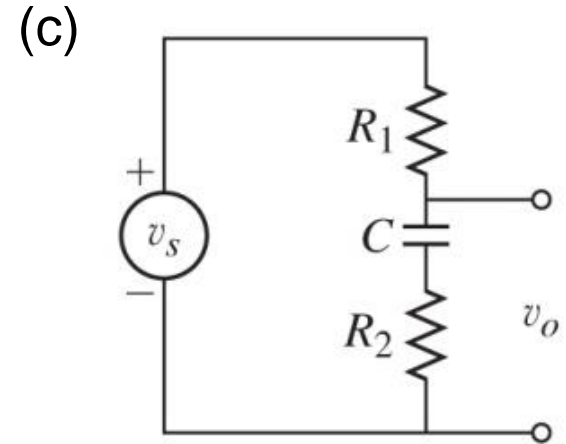
$$\frac{L}{R} \frac{dv_o}{dt} + v_o = \frac{L}{R} \frac{dv_s}{dt}$$




$$(R_1 + R_2)C \frac{dv_o}{dt} + v_o = R_2 C \frac{dv_s}{dt} + v_s$$

# Mathematical Modeling of Electrical Systems

## Example 4

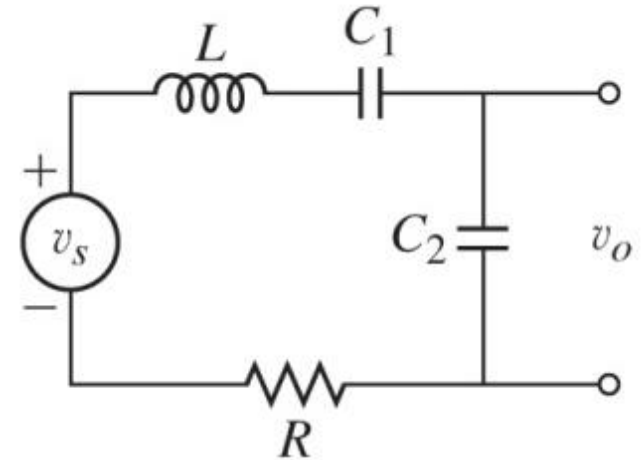
- a) Find the transfer function  $V_o(s)/V_s(s)$  of the electrical circuit below, given the supply voltage  $v_s$  and the output voltage  $v_o$ . Obtain the voltage  $v_o(t)$  when the input voltage  $v_s(t)$  is a impulse signal with strength of 10 V. Assume that initial conditions are zero, and that  $C_1 = C_2 = 10\mu F$ ,  $R = 200\ \Omega$ , and  $L = 2\text{ H}$



$$\frac{V_o(s)}{V_s(s)} = \frac{C_1}{LC_1C_2s^2 + RC_1C_2s + C_1 + C_2}$$

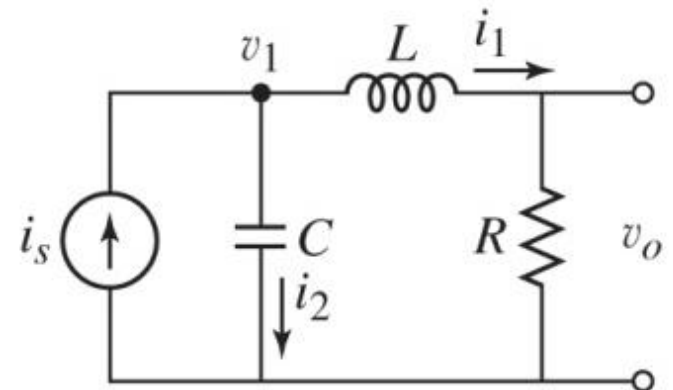- b) Obtain the state-space model of the circuit below, given the supply current  $i_s$  and the output voltage  $v_o$ .


$$LC \frac{d^2 v_o}{dt^2} + RC \frac{dv_o}{dt} + v_o = Ri_s$$



# Mathematical Modeling of Electrical Systems
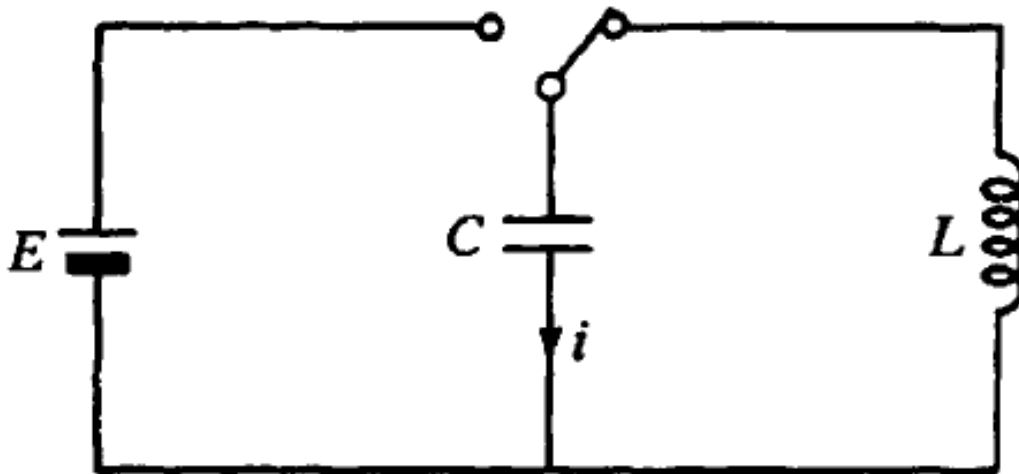
## Example 5

Consider the circuit shown in the Figure. Assume that capacitor  $C$  is initially charged to  $q_0$ . At  $t = 0$ , switch  $S$  is disconnected from the battery and simultaneously connected to inductor  $L$ . The capacitance has a value of  $50 \mu F$ . Calculate the value of the inductance  $L$  that will make the oscillation occur at a frequency of 200 Hz.



$$L = 0.0127 \text{ H}$$

$$L \frac{di}{dt} + \frac{1}{C} \int i dt = 0$$


$$L \frac{d^2 i}{dt^2} + \frac{1}{C} i = 0$$

$$L \frac{d^2 q}{dt^2} + \frac{1}{C} q = 0$$

# Mathematical Modeling of Electrical Systems
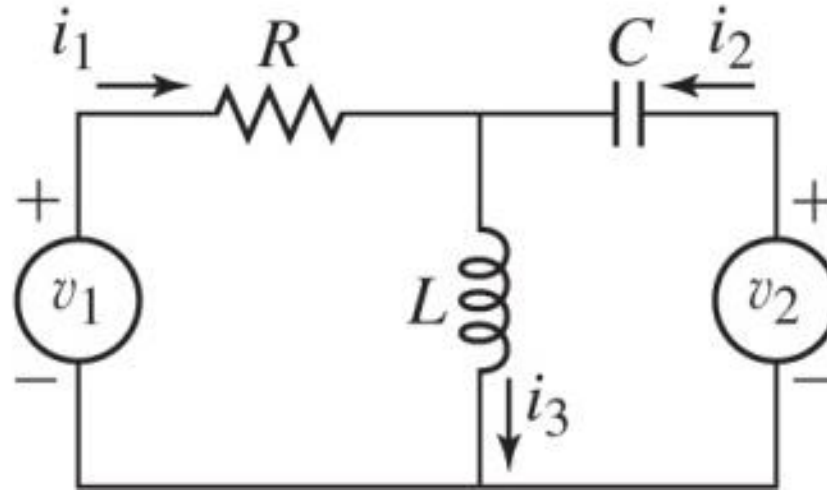
## Example 6

The  $RLC$  circuit shown in the Figure has two input voltages. Obtain the differential equation model for the current  $i_3(t)$ .




$$LRC \frac{d^2 i_3}{dt^2} + L \frac{di_3}{dt} + Ri_3 = v_1 + RC \frac{dv_2}{dt}$$

Obtain the current response  $i_3(t)$  using MATLAB/Simulink. The parameter values are  $R = 10^3 \Omega$ ,  $C = 2 \times 10^{-6} \text{ F}$ , and  $L = 2 \times 10^{-3} \text{ H}$ . The voltage  $v_1(t)$  is a step input of magnitude 5 V, and the voltage  $v_2(t)$  is sinusoidal with frequency of 60 Hz and an amplitude of 4 V. The initial conditions are zero.

# Mathematical Modeling of Electrical Systems
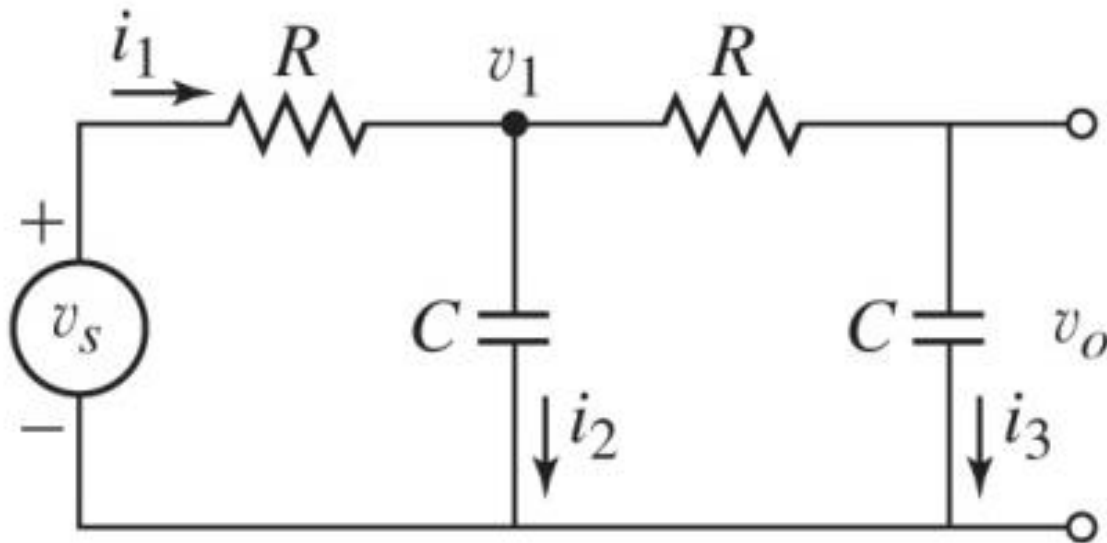
## Example 7

Determine the transfer function  $V_o(s)/V_s(s)$  of the circuit below, given the supply voltage  $v_s$  and the output voltage  $v_o$ . Draw two simulation block diagrams for the system.



$$\frac{V_o(s)}{V_s(s)} = \frac{1}{R^2 C^2 s^2 + 3RCs + 1}$$



# Mathematical Modeling of Electrical Systems

## Example 7

Find the transfer function  $V_o(s)/V_s(s)$  of the electrical circuit below, given the supply voltage  $v_s$  and the output voltage  $v_o$ . Draw two simulation block diagrams for the system.

